

DC-DC BOOST CONVERTER PROTOTYPE

For PV-Integrated Electric Vehicle (Scale-Down Prototype)

20W Solar Panel | 48V Battery Output | DC-DC Boost Converter Design
week 07

E21060 | BHASHINI A.J.
Department Of Electrical & Electronic Engineering
Faculty Of Engineering | Univesity Of Peradeniya

SOLUTION TIME STEP

In PSCAD, the solver works by taking snapshots of the circuit at fixed time intervals called the solution time step. It can only switch the MOSFET ON or OFF at these exact snapshot moments.

For a switching frequency of 20 kHz,

$$\text{switching period } T = 50 \mu\text{s}$$


For a duty cycle of $D = 0.6265$,

$$\begin{aligned}\text{Required ON-time} &= 0.6265 \times 50 \\ &= 31.325 \mu\text{s}.\end{aligned}$$


With the original solution time step of $0.5 \mu\text{s}$, the solver could not switch at exactly $31.325 \mu\text{s}$ — it rounded to the nearest available snapshot, resulting a small error in the actual duty cycle applied.

Since the boost converter output voltage is highly sensitive to duty cycle, even this small rounding error caused the output voltage to deviate from the 48 V target.

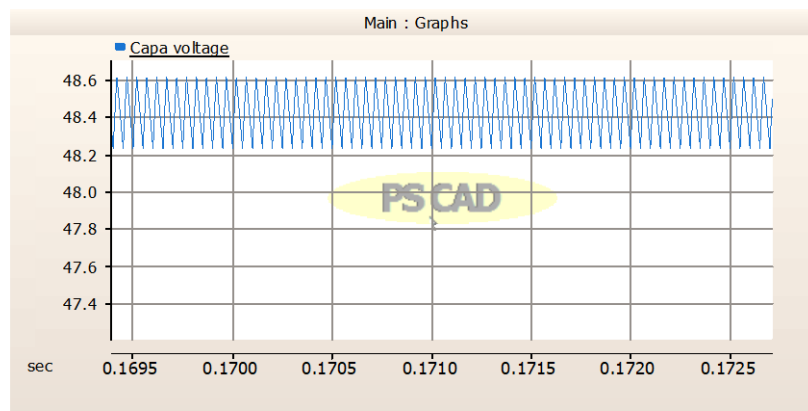
By reducing the solution time step to $0.315 \mu\text{s}$, the solver gained finer resolution and could represent the switching instant much more accurately, bringing the simulated output voltage to approximately 48 V as expected from the theoretical design.




0.2

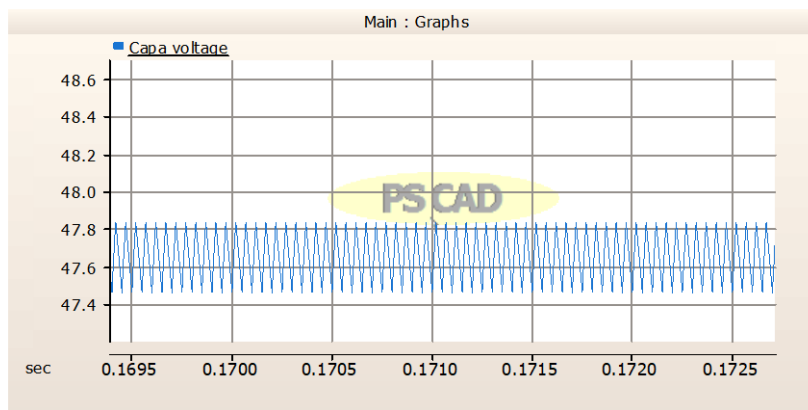

0.5

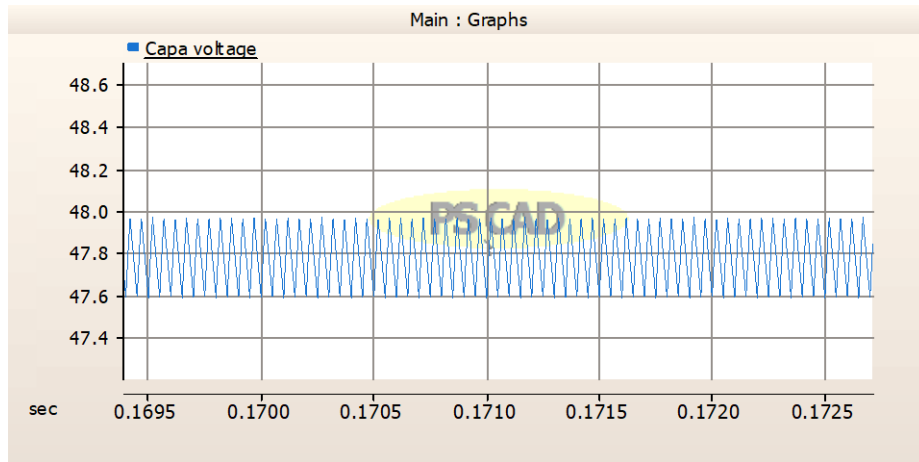

0.3125

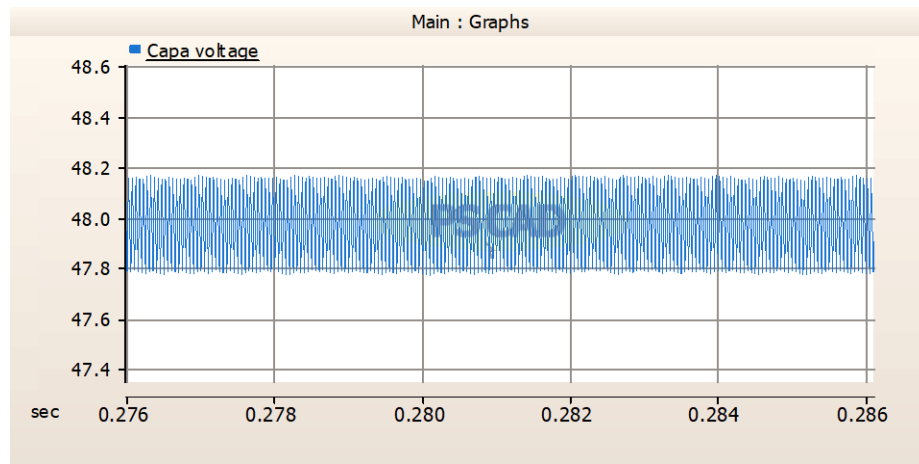

0.315

Time Step (μs)	Avg Vout (V)	Vout Ripple ΔV (V)	Ripple %
Designed value for 33 μF	48.00	0.396	0.82%
0.200 μs	47.65	0.30	0.63%
0.300 μs	47.80	0.33	0.69%
0.3125 μs	48.43	0.30	0.62%
0.315 μs	47.97	0.38	0.79%

CURRENT RIPPLE AND INDUCTOR

- At 30% ripple ,

$$\Delta I_L = 0.30 \times 1.115 = 0.3345 \text{ A}$$

The minimum inductance required to maintain Continuous Conduction Mode (CCM) is:

$$L_{min} = \frac{V_{in(min)} \cdot D_{max}}{\Delta I_L \cdot f_{sw}}$$


$$L_{min} = \frac{17.93 \times 0.6265}{0.3345 \times 20000}$$
$$= 1677 \text{ } \mu\text{H}$$

- At 20% ripple , $\Delta I_L = 0.20 \times 1.115 = 0.223 \text{ A}$

$$L_{max} = \frac{V_{in(min)} \cdot D_{max}}{\Delta I_L \cdot f_{sw}}$$

$$L_{max} = \frac{17.93 \times 0.6265}{0.223 \times 20000}$$
$$= 2519 \text{ } \mu\text{H}$$

- Inductance range: 1677 μH to 2519 μH

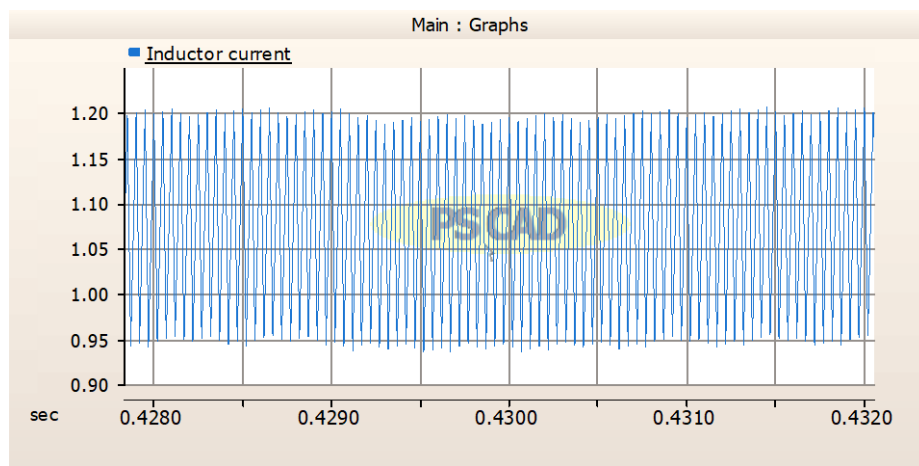

COMPONENT LIST

Component	Selected Part	Specification / Reason
Solar Panel	20W Poly/Monocrystalline	$V_{mp}=17.93V$, $I_{mp}=1.11A$, $P=20W$
MOSFET (Switch)	IRF540N	Rated 100V/28 A, low $R_{ds(on)}$
Diode	MBR10100CT Schottky	20A / 100V, fast switching, low V_f
Inductor	1.7 mH Toroidal	Rated $\geq 2A$, ferrite core, ensures CCM
Output Capacitor	33 μF / 100V Electrolytic	Smooth 48V output, 100V safety margin
Gate Driver	IR2110	Drives MOSFET gate from MCU PWM signal
PWM Controller	Arduino Uno	Generates 20 kHz PWM at 62.65% duty cycle
Load Resistor (Lab)	120 Ω / 25W Wirewound	Initial testing before battery connection